

HELLO
AND
WELCOME TO OUR
PRESENTATION

PRESENTED BY



Shafiul Islam Joy

ID:1702005



Antor Shaha

ID:1702006



Md. Hasibul Hasan Chowdhury

ID:1702007



Iasin Arafat

ID: 1702008


WE ARE
PRESENTING
ON
WATER LEVEL INDICATOR WITH
ALARM !!



INTRODUCTION


The water level alarm circuit is a simple mechanism to detect and indicate the level of water in the overhead tank and also in the other containers.

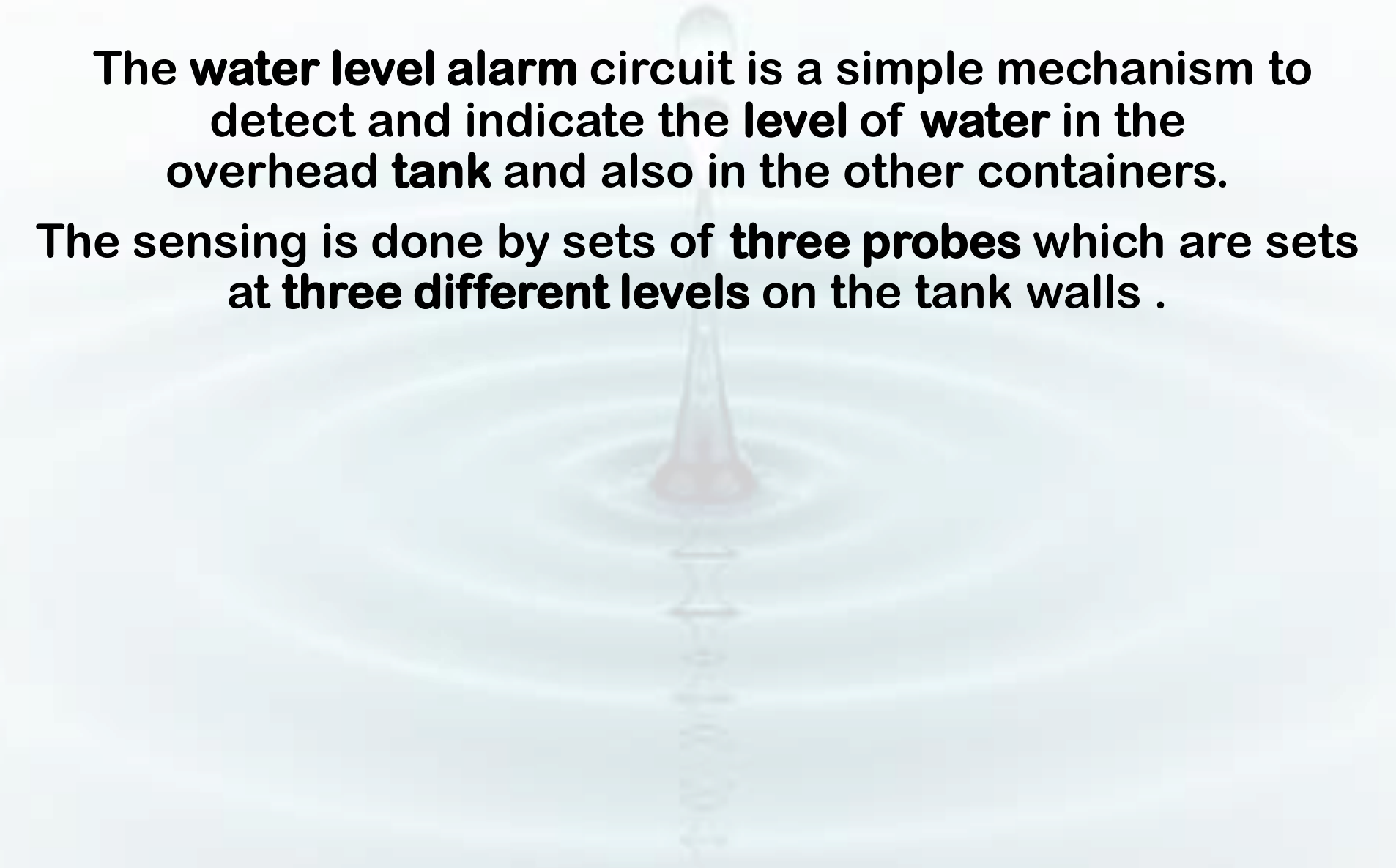The sensing is done by sets of three probes which are sets at three different levels on the tank walls .



COMPONENTS

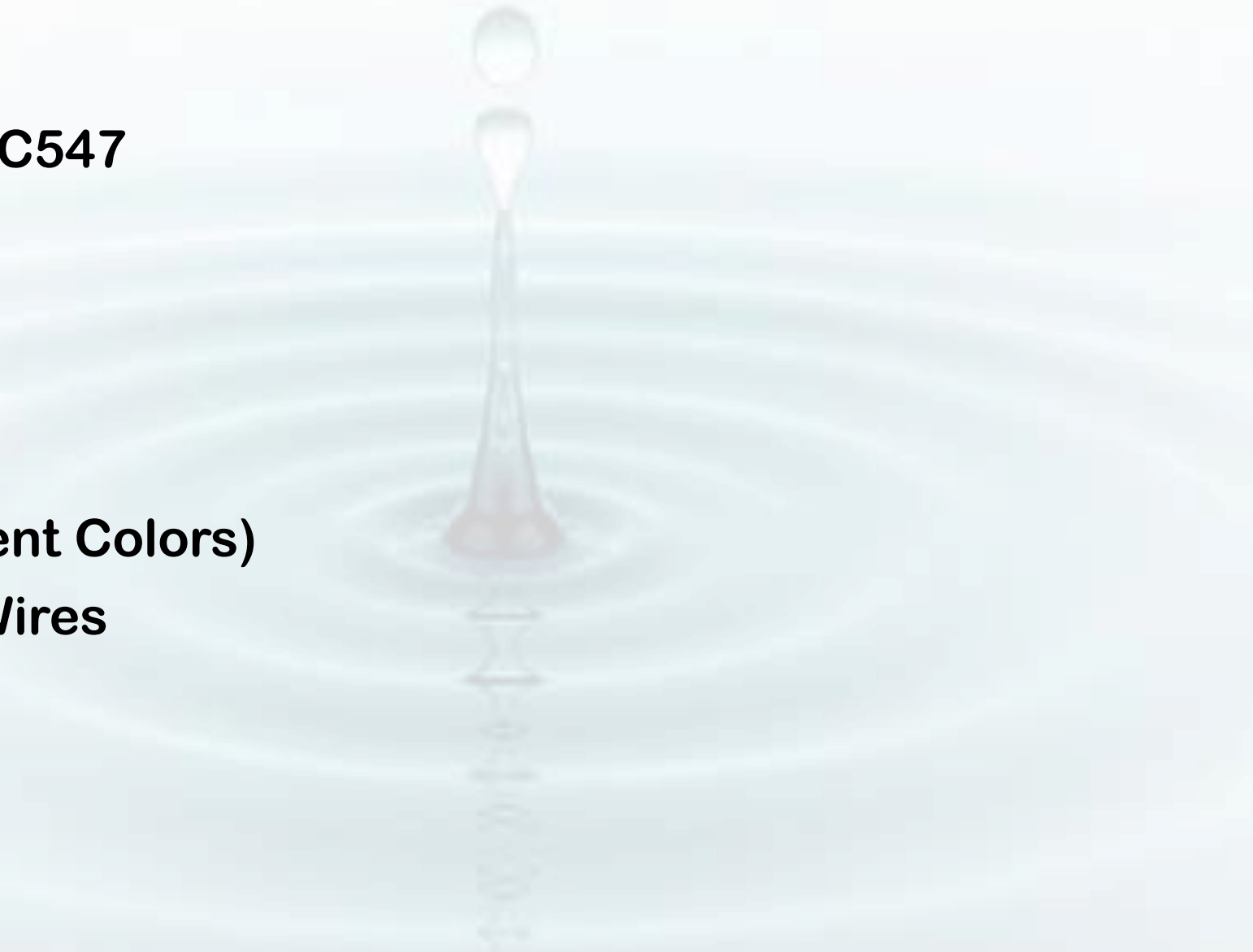
- Transistors BC547
- 150 Ω Resistor
- Buzzers/LED
- 9V supply
- Bread Board
- LED's (Different Colors)
- Connecting Wires



BRIEF NOTES OF SOME OF THE COMPONENTS WE USE

- **BREAD BOARD** :A board for making an experimental model of an electric circuit.
- **TRANSISTOR**: In this circuit we use BC547 transistor , which is very common emitter NPN transistor and its basically used for the amplification and switching purpose .
- **BUZZER** :It produces sound actual use for the alarm circuit.
- **LED** :A LED is a two lead semiconductor light source , is a p-n junction diode , emits light when activated

CIRCUIT DIAGRAM

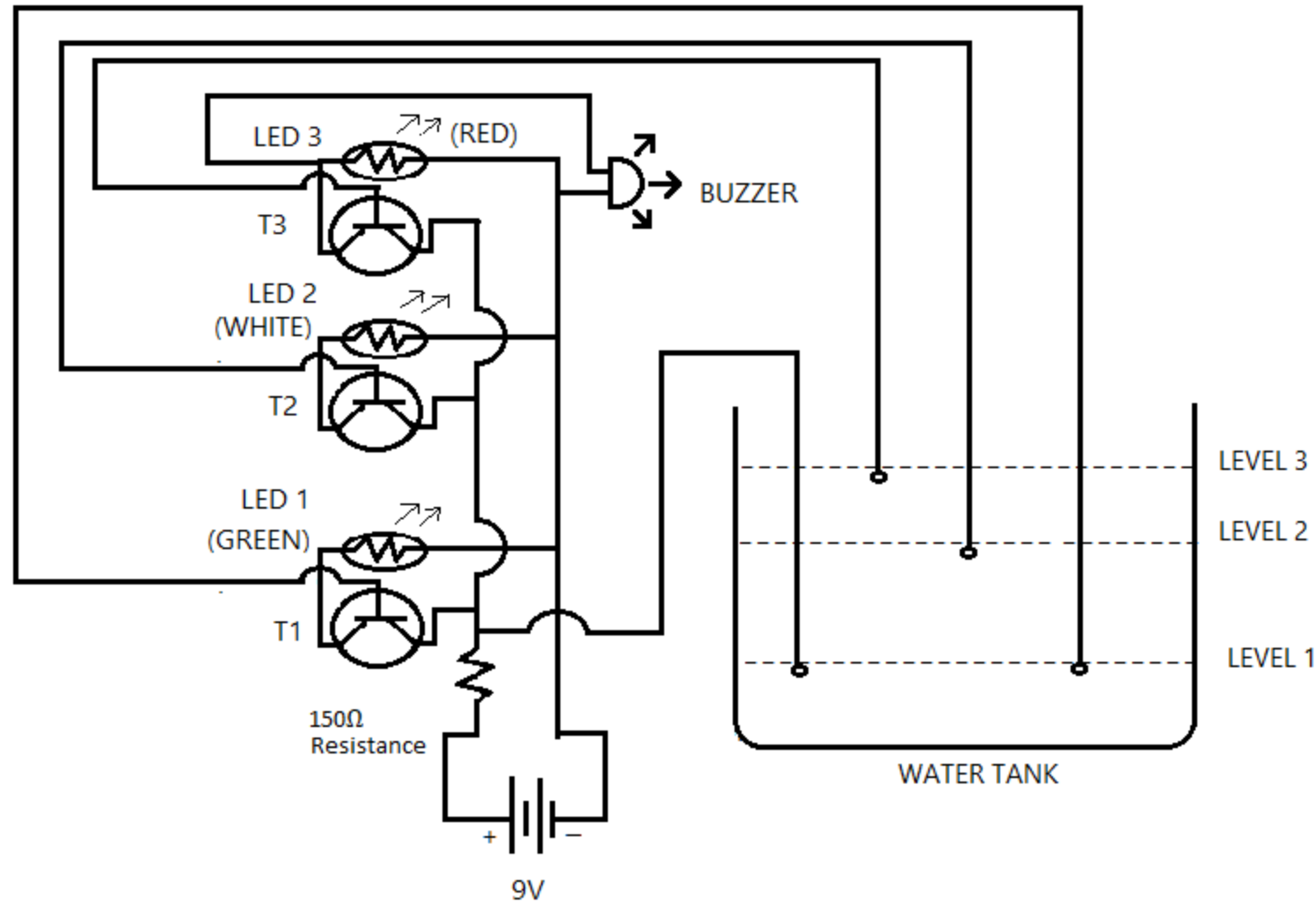

WORKING PRINCIPLE

- The operation of the project is very simple and can be understood very easily. In our project “ Water level indicator” there are three main conditions:
- There is no water or very less water available in the source tank. Intermediate level.
- There is ample amount of water available in the source tank or about to overflow.
- So let us discuss on the more about these three condition.

WORKING PRINCIPLE

- After establishing the the required connection as shown in the circuit diagram , we place the other ends of the three wires which are connected to the base of the three transistors into a bowl at three different levels of height.
- Suppose wire 1 is at a lower height.
- Wire 2 is at a medium height.
- Wire 3 is at a height from which water is supposed to overflow.

WORKING PRINCIPLE

- As we start pouring water into the bowl, the water level touches the first (wire 1) which is at a lower height and the circuit gets completed and currents starts flowing and the first LED (D1) glows.
- Gradually, as the level of water goes on increasing the other two LEDs
- (D2 and D3 glows) indicating that the water has reached to maximum height.
- As the water level crosses the maximum limit, the buzzer starts beeping and thus sends an alarm so that we can stop the supply of the water.
- Thus, this simple circuit depicts how a simple water level indicator help us in preventing the flow of water and further help us in reducing the wastage of water and power.
- So, it turns us to be very useful appliance which can used.

HAVE A LOOK



ADVANTAGES

- **Power Saver**
- **Money Saver**
- **Automatic**
- **Preventing wastage of water**
- **Reliable Electronic design**
- **Easy Installation with LED monitoring**

DISADVANTAGES

- **Water level controls need to be replaced every 3 years.**
- **The rust, foul and deteriorate**
- **Most float switches are outdated**
- **Unable to handle the high power**

APPLICATIONS AND IT'S USES

- Water tank level control
- Automatically turn ON/OFF pumps
- Can be used in factories, commercial complexes, apartments, home
- Fuel tank level gauging
- Oil tank level control
- Stream level monitoring
- Tsunami warning and sea level monitoring and many more.

TO SUM UP,

This is a simple model **water level indicator** which can be made at your home.

This project is the solution to help the user to indicate **water level** in reservoir or into the **water tank** that indicated different **levels** in an over head tank.

Finally the project has been successfully implemented and tested , the project gave us more confidence that we will be able to put it in a practice.

Remember,

“Technology is not just a tool , it can give learners a voice that they may not have had before”

THANK YOU ALL,
THAT'S ALL FOR NOW ,ANY QUESTIONS?

